

Digital Electronics - Internal Assessment - (4)

NAME: YASHVARDHAN SINGH

SEM: IIIRD


BRANCH: Electronics Engg.

ROLL No. : 46


REG. No. : 230959136

SIGN: Yue

 Q1] (i) 3 bit asynchronous up counter using T-ff




 (ii) 3 bit asynchronous down counter using T-ff




↪ uses positive edge triggered clock instead of the negative edge triggered clock being used by up-counter (asynchronous).

Q1] (iii)

 

3-bit asynchronous up counter

(iv)

 

3-bit asynchronous down counter

Q11
V


3 bit synchronous up counter using JK-FF.

Excitation table of JK:

Q_n	Q_{n+1}	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

yashvardhan Singh
VLSI-46
230959136
yvs

State-diagram:

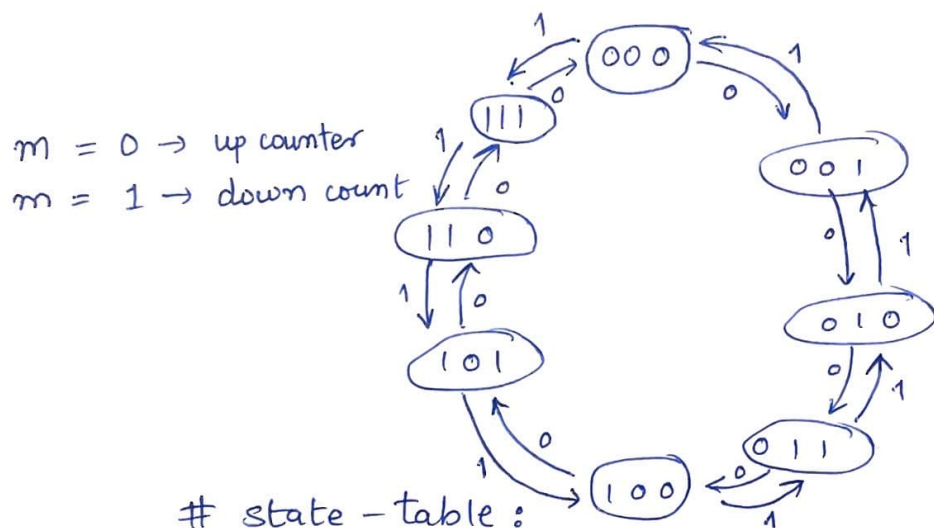


state-table:


m	Q_2	Q_1	Q_0	Q_2^+	Q_1^+	Q_0^+	J_2	K_2	J_1	K_1	J_0	K_0
UP { 0 0 0 0 0 0 0 0	0	0	0	0	0	1	0	x	0	x	1	x
	0	0	1	0	1	0	0	x	1	x	x	1
	0	1	0	0	1	1	0	x	x	0	1	x
	0	1	1	1	0	0	1	x	x	1	x	1
	0	0	0	1	0	1	x	0	0	x	1	x
	1	0	1	1	1	0	x	0	1	x	x	1
	1	1	0	1	0	0	x	1	x	0	1	x
	1	1	1	0	0	0	x	1	x	1	x	1
DOWN { 1 1 1 1 1 1 1 1	0	0	0	1	1	1	1	x	1	x	1	x
	0	0	1	0	0	0	0	x	0	x	x	1
	0	1	0	0	0	1	0	x	x	1	1	x
	0	1	1	0	1	0	0	x	1	x	1	x
	1	0	0	1	0	0	x	0	0	x	x	1
	1	0	1	1	0	1	x	0	x	1	1	x
	1	1	0	1	1	0	x	0	x	0	x	1
	1	1	1	0	0	0	x	0	x	1	x	1

⑤ # Solving k-maps : for (m = 0)

 
yashwardhan
Singh
VLSI - 46
230959136
yash




$$J_2 = Q_1 Q_0$$

 


$$J_1 = Q_0$$

 


$$J_0 = 1$$

 

$$K_2 = Q_1 Q_0$$

 

$$K_1 = Q_0$$

 


$$K_0 = 1$$

clock and state table:

	Q^+	\overline{Q}^+
→ +ve edge	down	up
→ -ve edge	up	down

circuit diagram:

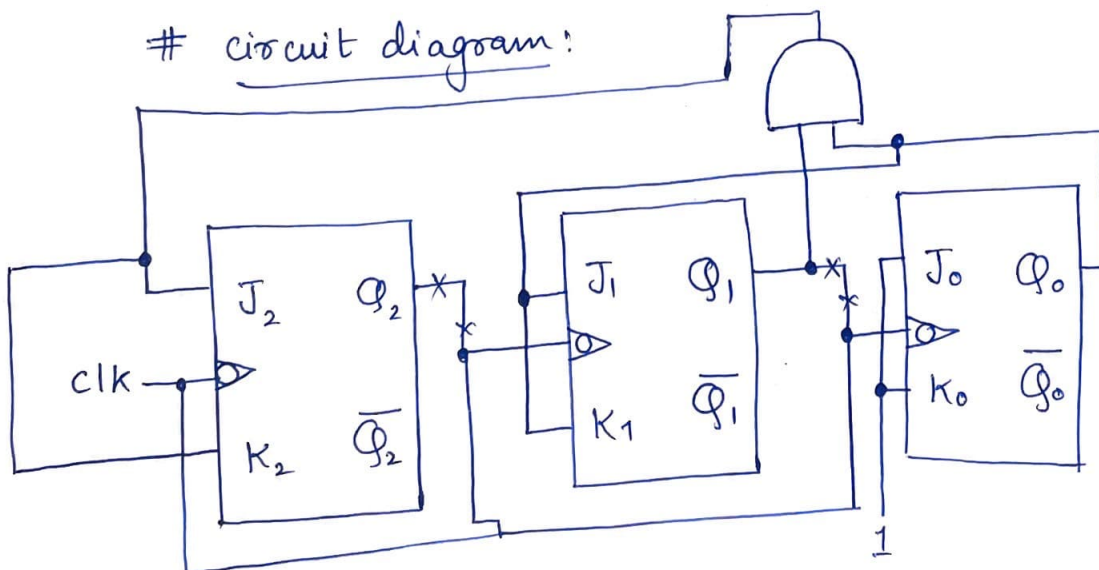

Q1] (VI) 3 bit synchronous down counter

→ borrowing the state table / diagram and excitation table from Q1. (V), for $m=1$.

yashwardhan singh
230959136
RHSI-46
yuv...

solving k-maps for $m=1$

J_1

$Q_2 \backslash Q_1 Q_0$	00	01	11	10
0	1	0	X ³	X ²
1	1	0	X ⁷	X ⁶

$J_1 = \overline{Q_0}$

K_1

$Q_2 \backslash Q_1 Q_0$	00	01	11	10
0	X ⁰	X ¹	0 ³	0 ²
1	X ⁴	X ⁵	0 ⁷	1 ⁶

$K_1 = \overline{Q_0}$

J_2

$Q_2 \backslash Q_1 Q_0$	00	01	11	10
0	1	0	0	0
1	X ⁴	X ⁵	X ⁷	X ⁶

$J_2 = \overline{Q_1} \overline{Q_0}$

K_2

$Q_2 \backslash Q_1 Q_0$	00	01	11	10
0	X ⁰	X ¹	X ³	X ²
1	1	0	0	0

$K_2 = \overline{Q_1} \overline{Q_0}$

$J_0, K_0 = 1 = \text{High}$


 


fig: 3 bit synchronous down counter

Q1] VII) 4 bit Johnson Counter :

 


TRUTH - TABLE :

clock	A	B	C	D
1	0	0	0	0
2	1	0	0	0
3	1	1	0	0
4	1	1	1	0
5	1	1	1	1
6	0	1	1	1
7	0	0	1	1
8	0	0	0	1


• after this cycle repeats...

VIII) 4 bit Ring Counter :

 


Q1] VIII) # Truth - Table:

clock	A	B	C	D
1	1	0	0	0
2	0	1	0	0
3	0	0	1	0
4	0	0	0	1
.... repeats				

 

→ please turn over...

yashwardhan singh
230959136
VLSI-46
yue

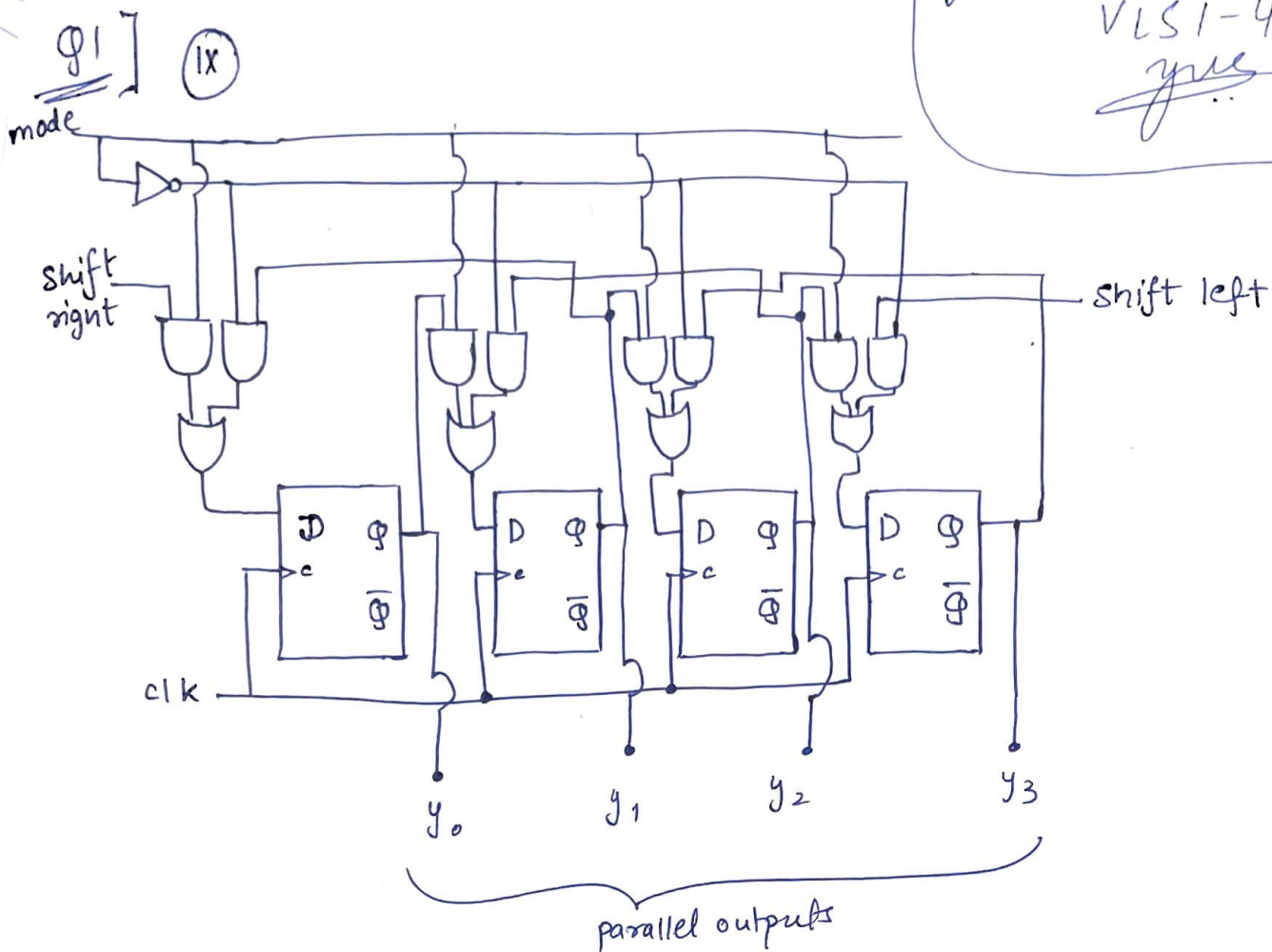

Bi-directional Shift Register

